

Labs 5 and 6: Latches, Flip-flops, and Synchronous Counters

ITI1100 A — Digital Systems I

Wassim El Ahmar

University of Ottawa

Emilien Breton — 300261694

Kiera Hutton — 300242006

April 8th, 2022

Lab 5: Latches and Flip-flops


Objectives

- Provide insight into the characteristics of several important latches and flip-flops.
- Build latches and flip-flops from basic gates.
- Explain concepts of latching and edge-triggering.
- Test latches and flip-flops to understand their operation.

Equipment and Components

- Quartus 11 13.0 Service Pack 1 (Local)

Part I — SR Latch

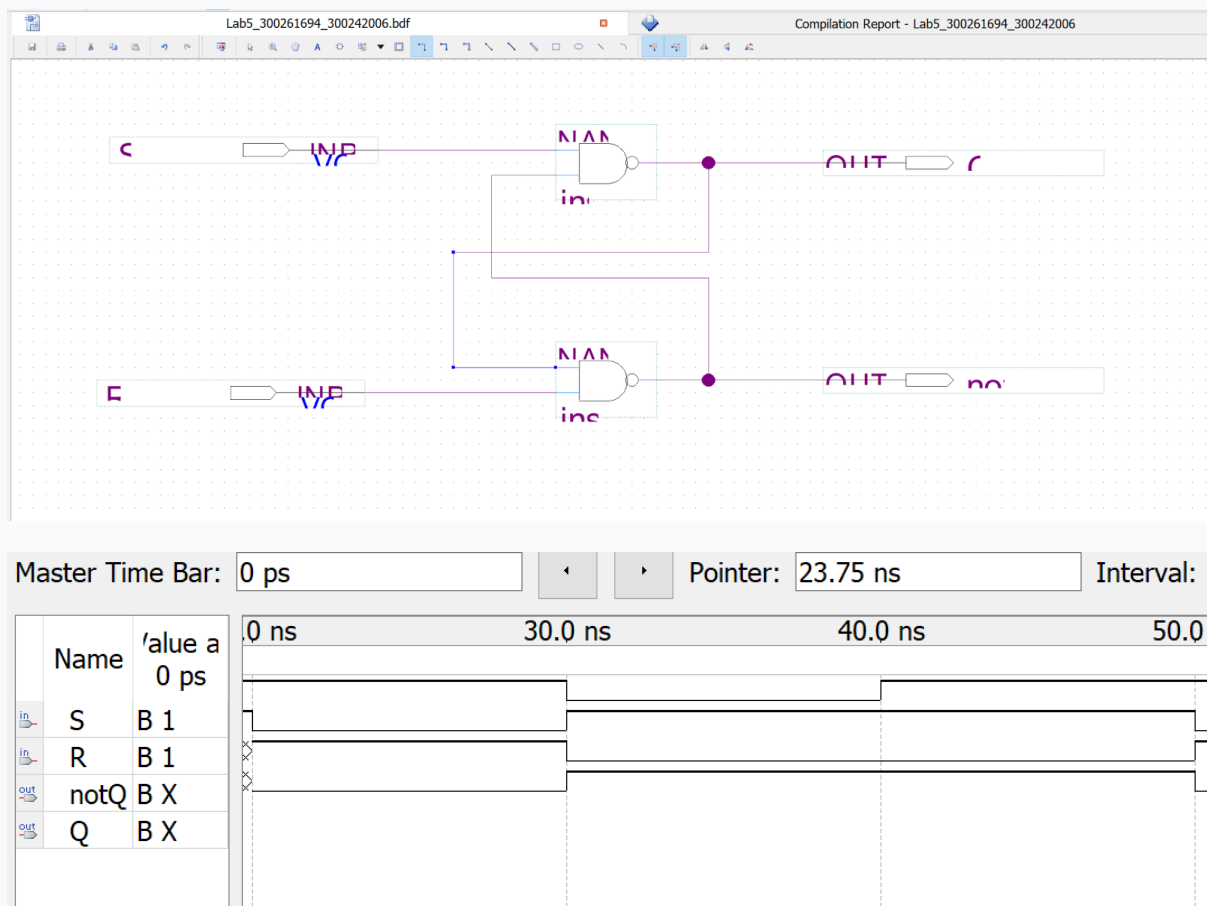



Experimental Function Table

S	R	Q_t	Q_{t+1}
1	1	\times	Q_t
1	0	\times	0
0	1	\times	1
0	0	\times	\times


Comparison of Expected and Experimental Data

Experimental data is identical to expected data.

Part II — D Latch

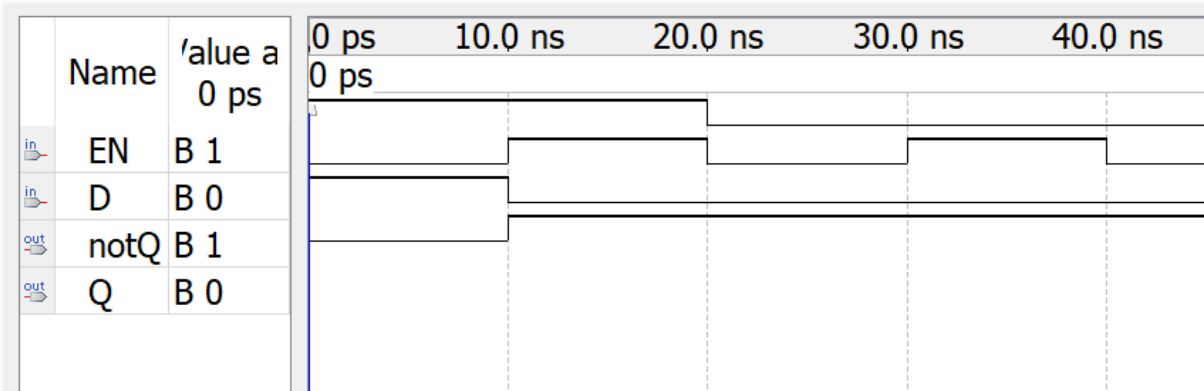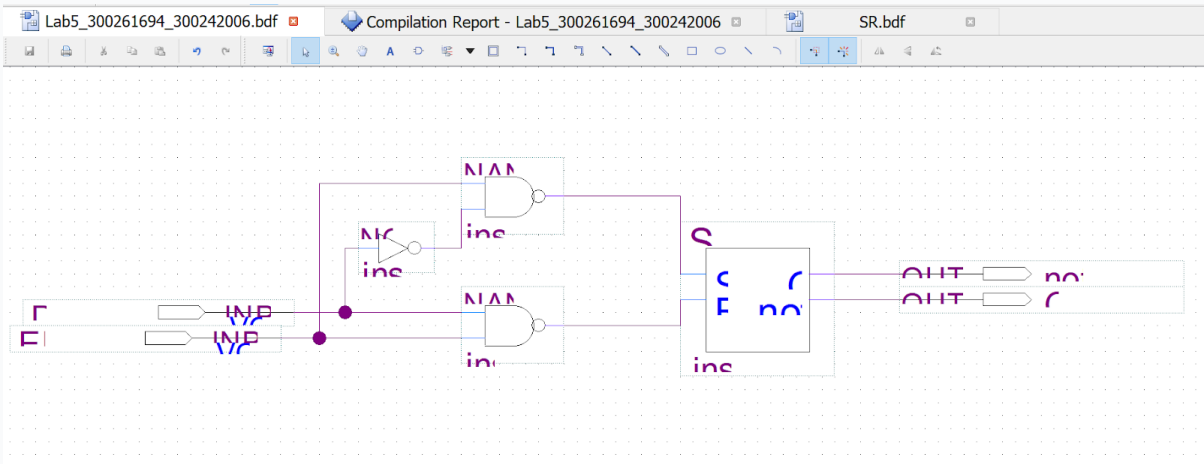

Part III — D Flip-Flop

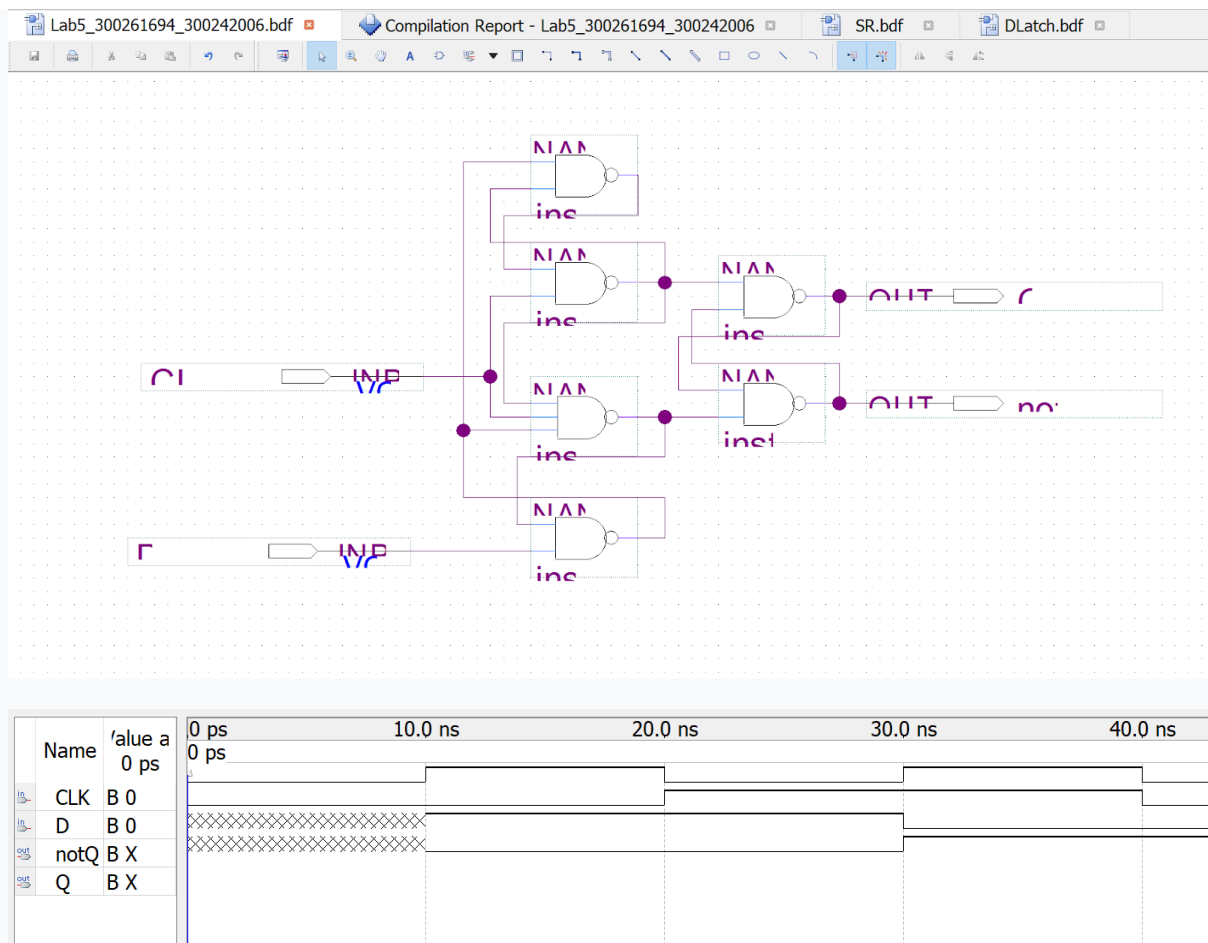


Experimental Function Table

CLK	D	Q_{t+1}	$\overline{Q_{t+1}}$
\uparrow	0	0	1
\uparrow	1	1	0
0	\times	Q_t	$\overline{Q_t}$
1	\times	Q_t	$\overline{Q_t}$

Comparison of Expected and Experimental Data

Experimental data is identical to expected data.

Part IV — T Flip-Flop

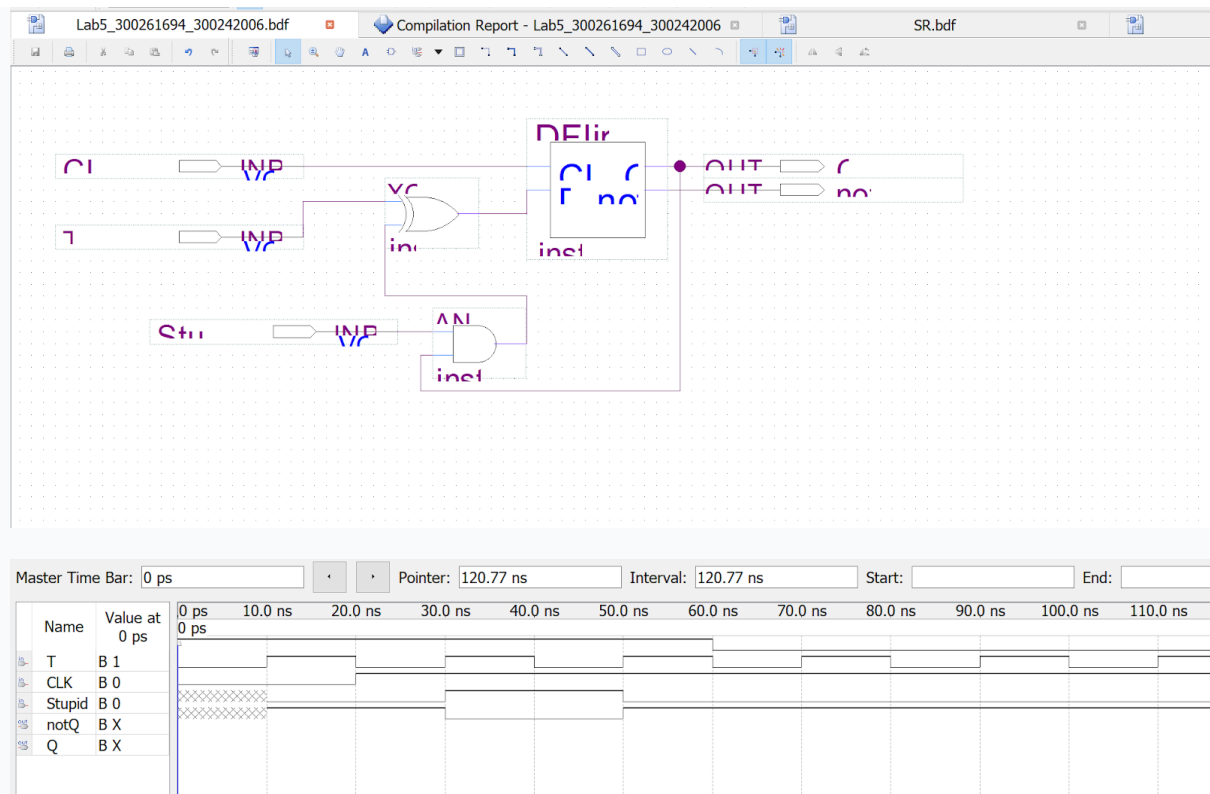

Experimental Function Table

CLK	D	Q_{t+1}	$\overline{Q_{t+1}}$
\uparrow	0	Q_t	$\overline{Q_t}$
\uparrow	1	$\overline{Q_t}$	Q_t
0	\times	Q_t	$\overline{Q_t}$
1	\times	Q_t	$\overline{Q_t}$

Comparison of Expected and Experimental Data

Experimental data is identical to expected data.

Discussion and Conclusion

In this laboratory, we created several logic circuits using Quartus. We then analysed the circuits to predict their operation. Finally, we simulated the circuits to make sure our theoretical predictions were the same as the experimental results.

The experimental and expected data matched completely. We met the objectives of building latches and flip-flops from basic gates, and testing the latches and the flip-flops to understand their operation by creating and testing the following:

- SR Latch
- D Latch
- D Flip-Flop
- T Flip-Flop

Challenges

- We had to use an outdated version of Quartus for the labs, which often breaks for no apparent reason. The errors we received were unrelated to the actual issues in our circuits, making debugging very annoying.
- We had to use a manual reset signal for **Part III** as Quartus would set all outputs to `undefined` otherwise.
- It was unclear whether the gates used had to be active high or active low.

Lab 6: Synchronous Counters


Objectives


- Design synchronous counters
- Simulate the functions of the various counters in this laboratory exercise

Equipment and Components

- Quartus 11 13.0 Service Pack 1 (Local)

Part I

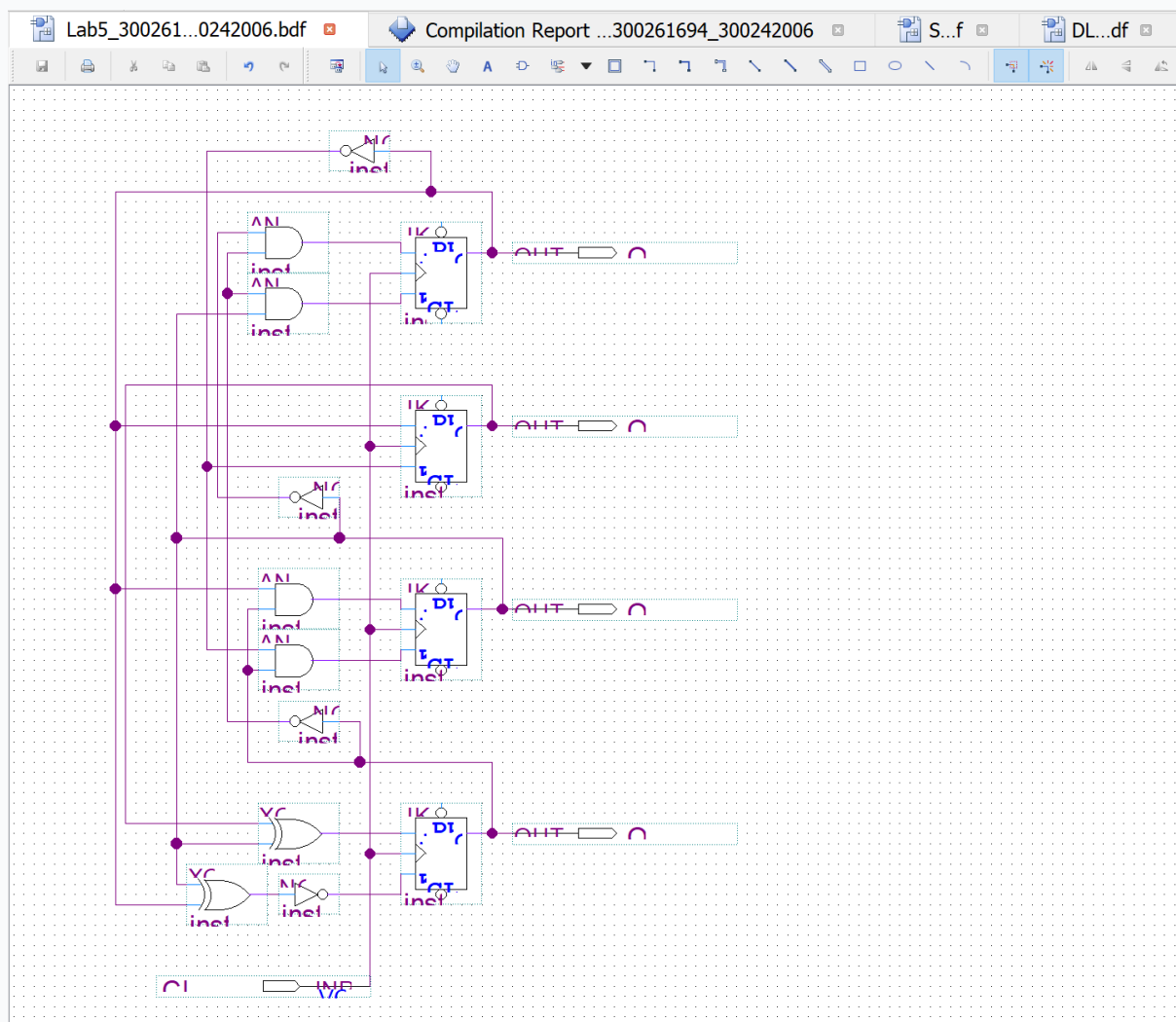

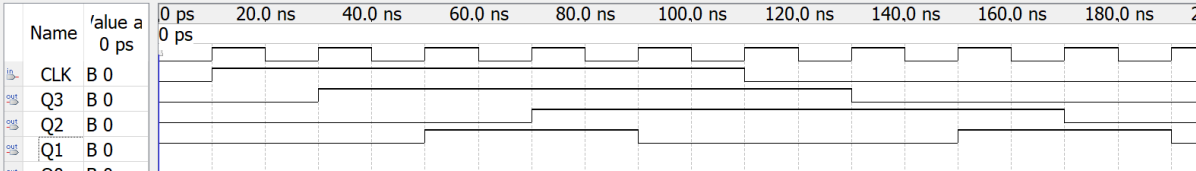


Experimental Function Table

<i>CLK</i>	<i>Q_t</i>	<i>Q_{t+1}</i>
↑	0	8
↑	8	12
↑	12	13
↑	13	15
↑	15	14
↑	14	6
↑	6	2
↑	2	3
↑	3	1
↑	1	0
0	×	<i>Q_t</i>
1	×	<i>Q_t</i>

Comparison of Expected and Experimental Data

Experimental data is identical to expected data.

Part II

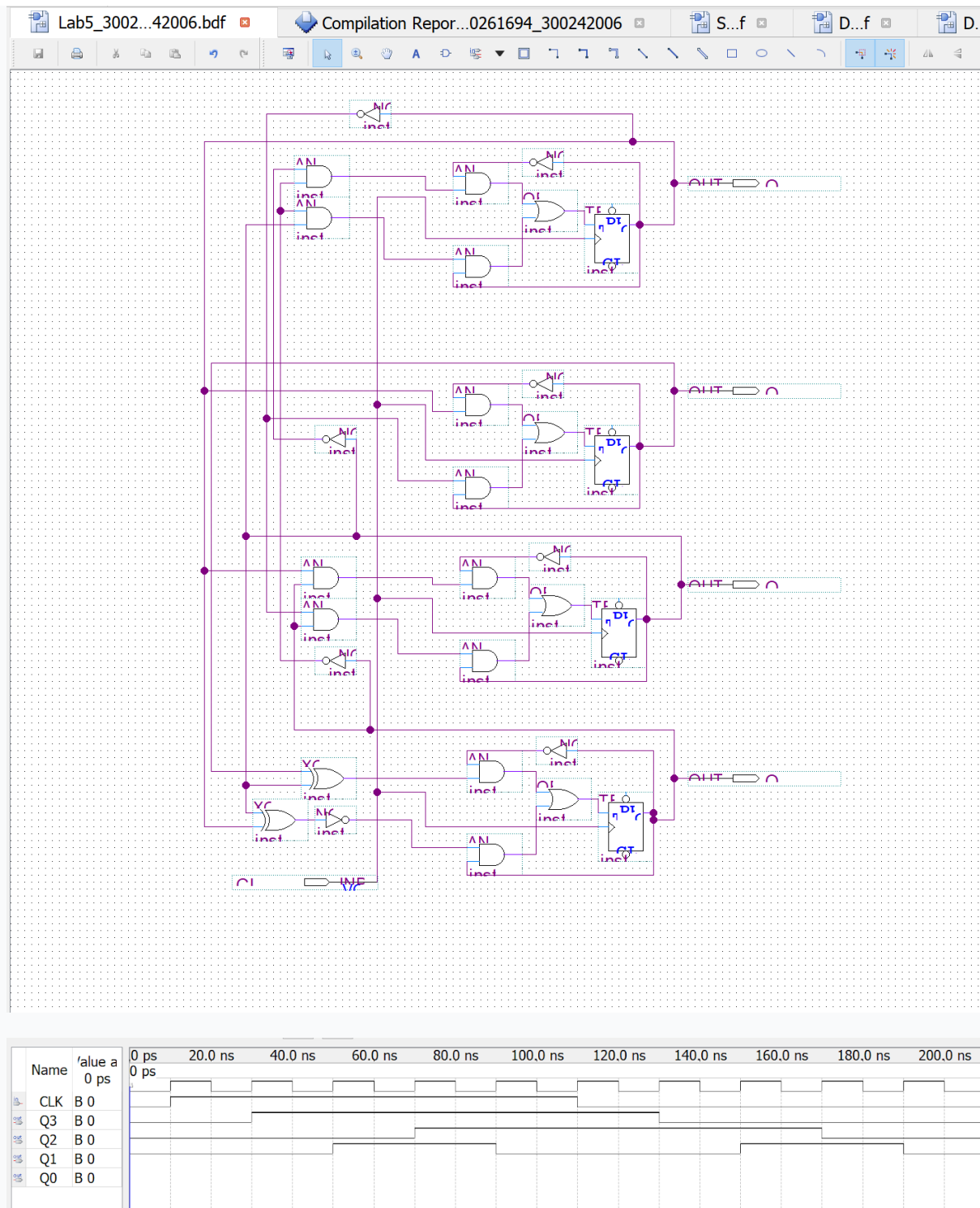

Comparison of Expected and Experimental Data


Experimental data is identical to expected data.

Discussion and Conclusion

In this laboratory, we created several logic circuits using Quartus. We then analysed the circuits to predict their operation. Finally, we simulated the circuits

to make sure our theoretical predictions were the same as the experimental results.

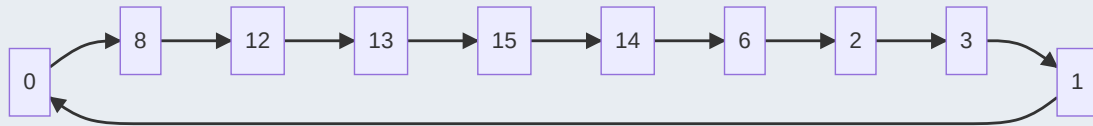The experimental and expected data matched completely. We met the objectives of designing synchronous counters and simulating the functions of the various counters by designing counters iterating through the following numbers:



Challenges

- We had to use an outdated version of Quartus for the labs, which often breaks for no apparent reason. The errors we received were unrelated to the actual issues in our circuits, making debugging very annoying.